

Project-I

EE619A

03/Mar/2025

1 Design Specifications

You are tasked with designing a backend for a mixed-signal IC as shown in Fig.1. Only the signals relevant to the backend design are shown here.

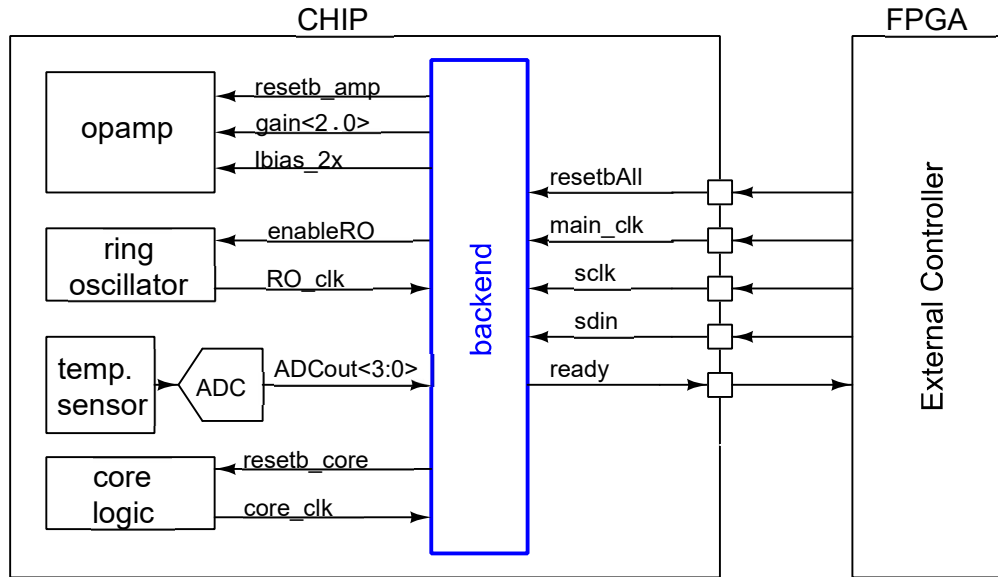


Figure 1: Overall block diagram.

The chip consists of an opamp, a ring oscillator, a temperature sensor, an ADC, a core logic and a backend. The backend has to ensure that all these analog modules are initialized correctly, and the chip is ready for use. The backend has to execute a start-up sequence for this, the details of which are given in Section 1.2. The chip will be interfaced with an external controller (most likely an FPGA) to control the start-up sequence. The outputs from the temperature sensor + ADC can be used to determine the temperature of the chip allowing to determine if the chip is in fast or slow conditions. If the chip is under slow conditions the bias current for the opamp needs to be doubled by setting $lbias_2x=1$. Under the slow conditions, the core logic will also need to be operated at a slower clock. The algorithm for doing this is also explained in Section 1.2.

1.1 Inputs and Outputs

The input and output pins of the backend are shown in Fig.2, along with the nets that will be connected to these pins at the top-level.

Inputs

- **i_resetbALL** : Active low reset for the whole chip. When $i_resetbALL = 0$, the backend and other analog modules will be reset. When $i_resetbALL$ goes from 0 to 1, startup sequence is initiated.
- **i_clk** : Main clock provided to the backend. Frequency: 500MHz.
- **i_sclk** : Clock provided for serial communication with the backend. Used to synchronize the programming data coming in through the i_sdin pin. i_sclk remains 1 when not in use. i_sclk , toggles like a clock when data is being sent from FPGA to the chip through i_sdin .

- **i_sdin** : Serial data input pin. FPGA will send 1 bit data at a time to the chip, to configure the gain of the opamp.
- **i_RO_clk** : The ring oscillator output. From simulations across PVT, the frequency of the ring oscillator can be anywhere within a range of 500MHz to 1.5GHz. i_RO_clk remains 0, when o_enableRO is 0.
- **i_ADCout<3:0>** : The temperature sensor output digitized using an ADC. The ADC output will range between 0 to 15.

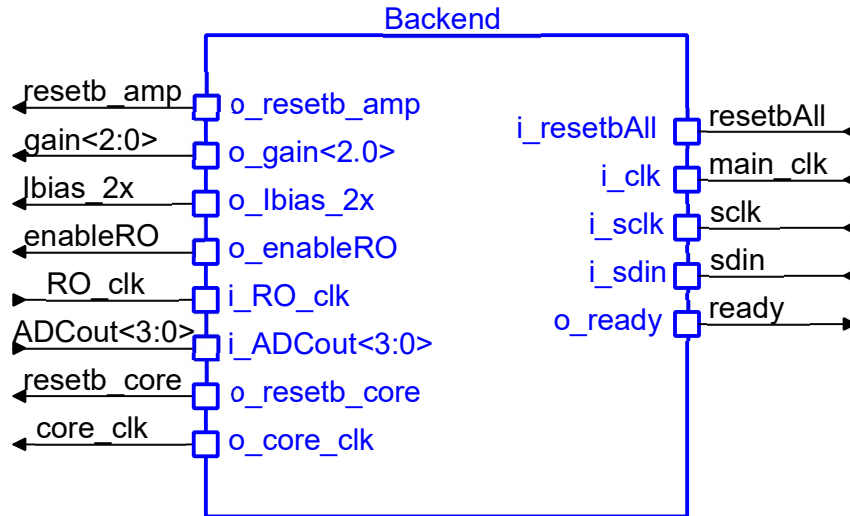


Figure 2: Input output configuration of the backend.

Outputs

- **o_ready** : When o_ready is 1, it indicates that the start-up sequence has been completed successfully and the amplifier and the core logic within the chip are ready to be used.
- **o_resetb_amp** : Active low reset for the opamp.
- **o_gain<2:0>** : Three bit value that controls the gain of the opamp.
- **lbias_2x** : Controls the bias current in the opamp. If lbias_2x is 1, the bias current in the opamp is doubled.
- **o_enableRO** : Active high enable signal for the ring oscillator.
- **o_resetb_core** : Active low reset for the logic core.
- **o_core_clk**: Clock to the logic core.

1.2 Backend functionality - start-up sequence

Please design the backend so that it executes the following start-up sequence.

1. When i_resetbAll = 0, all outputs of the backend should be pulled to 0. All internal registers should be either set or reset.
2. When i_resetbAll becomes 1, the start up sequence is initiated. The following instructions have to be executed in the given order.
3. Wait for the serial data from i_sdin. Read the data in. Details of this serial communication is explained in the Section 1.3.
4. Based on the serial data received, set the value of o_gain (refer Section 1.3).
5. Set o_enableRO=1.

6. Wait for five `i_clk` cycles.
7. The ADC output is to be filtered through a 4-tap moving average filter as shown in Fig. 4. While this is expected to be operating at all times, its outputs when `i_resetbAll=0` is not relevant. Implement the filter as a part of the backend. If the `ADCavg ≤ 12`, set `o_lbias_2x=0` and `o_core_clock=i_clk`. If the `ADCavg > 12`, set `o_lbias_2x=1` and `o_core_clock=i_clk/4` (frequency division). The state of the `o_core_clk` prior to this does not matter.
8. Set `o_resetb_amp=1` and `o_resetb_core=1`.
9. Wait for five clock cycles.
10. Set `o_ready=1`.
11. Keep monitoring the `ADCavg` signal. If `ADCavg` goes above 12, set `o_lbias_2x=1` and `o_core_clock=i_clk/4`. If `ADCavg` goes below 8, set `o_lbias_2x=0` and `o_core_clock=i_clk`. If $8 \leq \text{ADCavg} \leq 12$ retain the values of `o_lbias_2x` and `o_core_clk` as is. All other output values are to be held as is till the next falling edge of `i_resetbAll`.

1.3 Serial data communication

To configure the gain of the amplifier, overall 3-bit information is required. Instead of dedicating three pins for these, we send the data serially, one bit at a time. This technique is often used to reduce the number of pins required on the chip.

 


Figure 3: Serial data transmission using `sclk` and `sdin` lines.

The external controller will send the five programming bits after `i_resetbAll` is deasserted. The data transmission will be as shown in Fig.3. The FPGA will send the data at the falling edge of `sclk`. The backend has to receive these at the rising edge of `sclk`. The data corresponding to the first `sclk` cycle is `d0`, second `sclk` cycle is `d1` and so on. You can use a shift register configuration to read the `sdin`. `d0` to `d4` are related to the amplifier gains as follows.

- `o_gain<2:0> : {d2, d3, d4}`
- `d0` and `d1` are extra bits that may be used in the future. Not relevant to the current design.

Please note the order. `o_gain<2>` is `d2`, `o_gain<1>` is `d3` and so on. The `sclk` frequency is expected to be lower than 10MHz. The exact frequency of `sclk` is not known at the time of design.

1.4 Moving average filter for the ADC output

The implementation of the 4-tap moving average filter is shown in fig. 4. z^{-1} refers to one clock cycle delay. The filter ensures that momentary glitchy outputs in the sensor does not affect our decision making. You may use any of architecture for the adder and the multiplier. If you are able to optimize the filter implementation in terms of reducing the number of bits required for each operation you are free to do so, as long as the final transfer function from `ADCout` to `ADCavg` remains the same as shown in fig. 4.

 


Figure 4: Serial data transmission using sclk and sdin lines.